


CSE251: ASSIGNMENT-1

Full Marks: 70

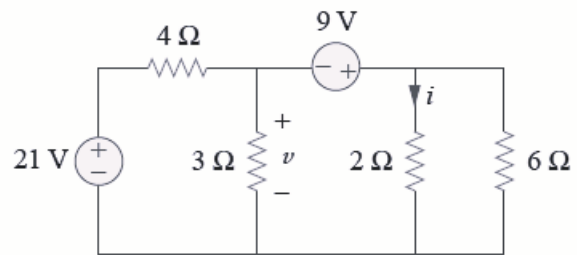Q1. [CO2]


10

- Draw** the alternative representation of circuit-1 .
- Analyze** the Circuit from question-1 to determine v and i .



Circuit-1

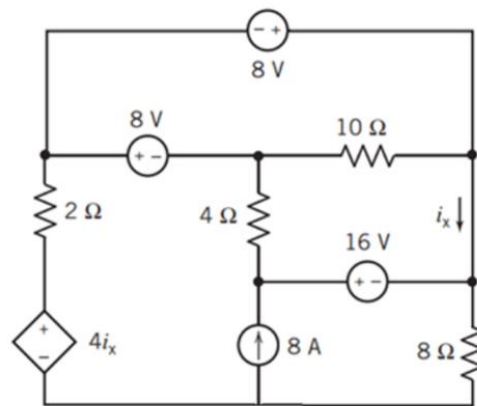
- Draw** an alternative representation of circuit-2 minimizing the number of floating voltage sources.



Circuit-2

Q2. [CO2]

10

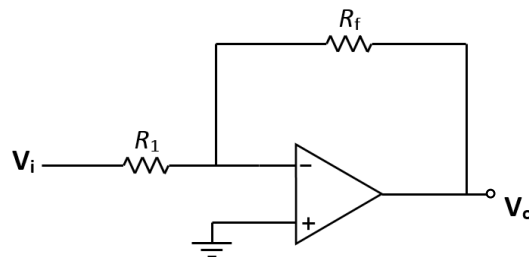


Circuit-3

For the circuit shown above , $R_1=2k$, $R_f=6k$, $+V_s=+15v$, $-V_s=-15v$

- Find** the value of V_o if $V_i=4v$
- Draw** the graph of V_o with proper labels if $V_i=4\sin(\omega t)$
- Draw** the graph of V_o with proper labels if $V_i=6\sin(\omega t)$

Q3. [CO2]

10

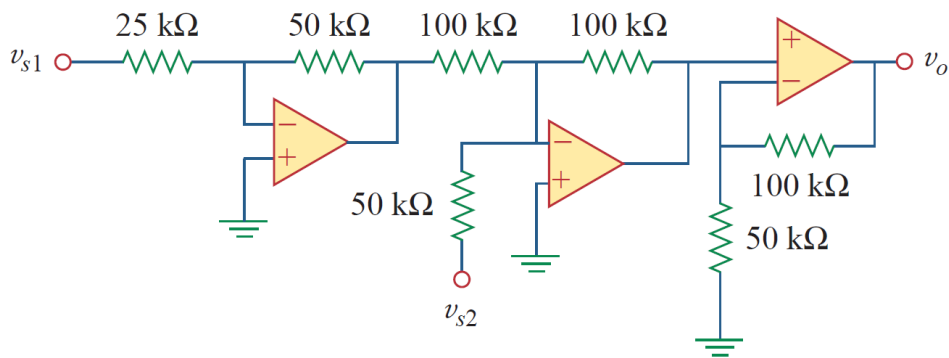


Analyze Circuit to Find V_o in terms of input V_{s1} and V_{s2} .

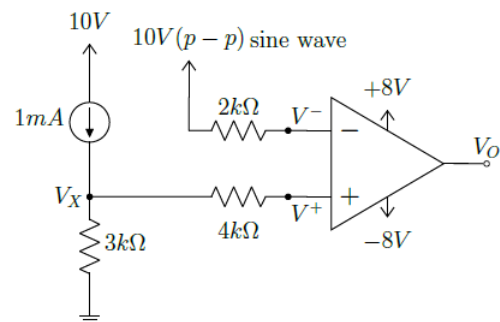Q4. [CO2]

10

Analyze the circuit to find V_x . Draw the waveform of V_o and label the graph properly.



Q5. [CO3] Design a circuit using OP-Amp to implement the following functions

10

- $f = 6x - 5y + z$
- $f = 5x - 10 \frac{dy}{dt} + 2 \int z dt$

Q6. [CO3]

5

Design a Circuit using OP-Amp that follows the voltage transfer characteristics (VTC) shown in figure-01

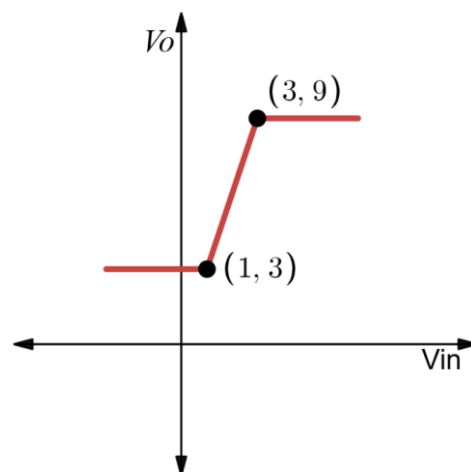


Figure 01

Q7. [CO3] Design a circuit using OP-Amp that takes V_{in} as the input and generates V_{out} as illustrated in Figure-2

10

- I. Design the circuit using inverting amplifier .
- II. Design the circuit using non-inverting amplifier .

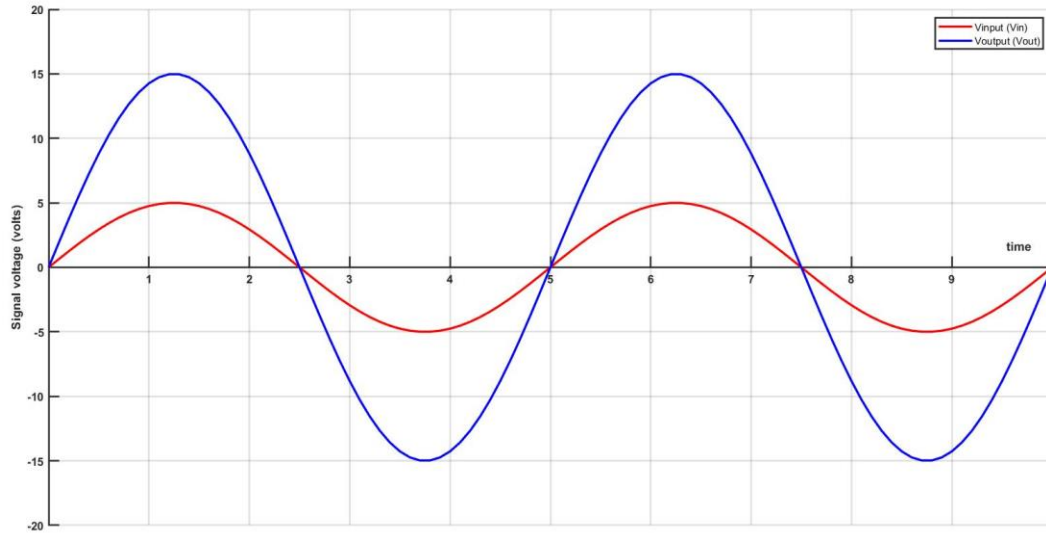


Figure 02

Q8. [CO3] Design a circuit using OP-Amp to generate the output V_{out} from the input V_{in} as illustrated in figure-3 .

5

[Hint: use summing amplifier]

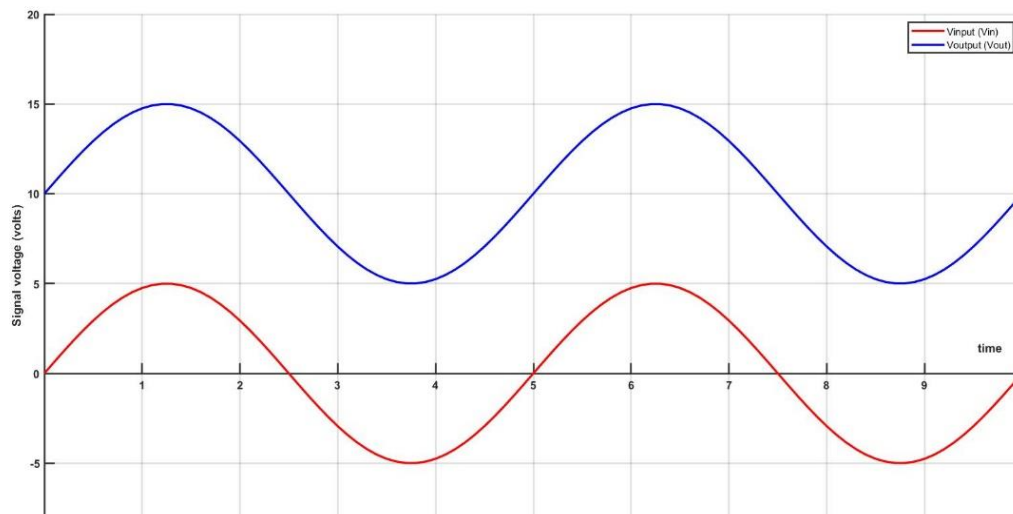


Figure 03